

## CHARGE & CURRENT

$v = \text{charge vel.}$	$Q_v = \text{charge density}$
$I = \frac{dq}{dt} = \lim_{\Delta t \rightarrow 0} \frac{\Delta Q}{\Delta t} = \frac{Q}{t}$	$A = \text{crosssection} \perp \text{to } I$
$\frac{Q}{L} = \frac{Q_v v}{L} = \frac{Q_v A L V}{L} = Q_v A V$	$t = \frac{L}{v}$
$I = \frac{Q}{t} = Q_v A v$	$q(t) = \int_0^t i(t') dt'$

## PIV, R CONVERSIONS

$$V = IR \quad I = V/R \quad R = V/I$$

$$P = IV = I^2 R = V^2/R$$

## DERIVATIVE DEFINITIONS

$$I = \frac{dq}{dt} \quad q = \int_{-\infty}^t i(t') dt$$

$$V_{AB} = \frac{dw}{dq}, (\text{dw: energy in J to move } t \text{ from b to a})$$

$$P = \frac{dw}{dt} = \frac{\delta W}{\delta t} \cdot \frac{dq}{dt} = VI$$

## TRAVELING WAVES

$$A \cdot \sin(kx \pm wt)$$

$$k: \text{wave vector} = 2\pi/\text{wavelength}, \lambda = \omega/2\pi \quad [\text{rad/m}]$$

$$\omega: \text{angular frequency} = 2\pi/\text{period} = 2\pi f \quad [\text{rad/s}]$$

$$v: \text{phase velocity} = \omega/k = \lambda f \quad [\text{m/s}]$$

## STANDING WAVES

$$\text{most general: } f(x, t) = A(\sin(kx - \omega t) - B(\sin(kx + \omega t))$$

$$= A[\sin(kx) \cos(\omega t) - \cos(kx) \sin(\omega t)]$$

$$+ B[\sin(kx) \cos(\omega t) + \cos(kx) \sin(\omega t)]$$

$$\text{salahuddin special: } f(x, t) = A[\sin(kx) \cos(\omega t) - \cos(kx) \sin(\omega t)]$$

$$\star x=0 \Rightarrow 0 = A[\sin(kx) \cos(\omega t)]$$

$$\star (x=L \Rightarrow 0) \Rightarrow k = \frac{n\pi}{L} = A[\sin(\frac{n\pi}{L} x) \cos(\omega t)], n \in \mathbb{Z}$$

$$1\text{st harmonic}$$

$$2\text{nd harmonic}$$

$$3\text{rd harmonic}$$

$$n\text{th harmonic mode } k_{n-1} = \frac{n\pi}{L}$$

$$\text{harmonic node, } n: \lambda = 2L/n$$

## MOBILITY & RESISTIVITY

$$\text{conductivity, } \sigma = n q_m$$

$$\text{resistivity, } \rho = \frac{1}{\sigma} = \frac{1}{n q_m}$$

$$\text{resistance, } R = \rho L/A$$

$$\text{mobility, } \mu = q T_{\text{avg}} / m_e$$

$$F = ma \rightarrow E_q = m \frac{d}{dt} T_{\text{avg}}$$

$$\rightarrow E_q T_{\text{avg}} / m = v$$

$$E = \text{electric field (V/m)}$$

$$v = \text{drift v of e (m/s)}$$

$$Q_v = \text{charge density}$$

## UNITS

$$\text{resistance } R \Omega \quad \text{time const. } \tau \text{ s}$$

$$\text{tera T } 10^{12} \quad \text{resistivity } \rho \text{ S/m}$$

$$\text{giga G } 10^9 \quad \text{conductance } G \text{ S}^{-1}$$

$$\text{mega M } 10^6 \quad \text{conductivity } \sigma \text{ S/m}$$

$$\text{kilo K } 10^3 \quad \text{impedance } Z \Omega$$


$$\text{milli m } 10^{-3} \quad \text{capacitance } C \text{ F}$$

$$\text{micro } \mu 10^{-6} \quad \text{inductance } L \text{ H}$$

$$\text{nano n } 10^{-9} \quad \text{mobility } \mu \text{ m}^2/\text{Vs}$$

$$\text{pico p } 10^{-12} \quad \text{charge den. } \rho \text{ C/m}^3$$

## CURRENT DIVISION

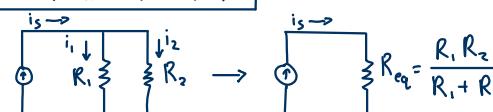

$$i_1 = \left( \frac{R_2}{R_1 + R_2} \right) i_s \quad i_2 = \left( \frac{R_1}{R_1 + R_2} \right) i_s$$

## VOLTAGE DIVISION



$$V_1 = \left( \frac{R_1}{R_1 + R_2} \right) V_s \quad V_2 = \left( \frac{R_2}{R_1 + R_2} \right) V_s$$

\*\* vs. only I sources

\* when there are only independent V sources

## NODAL ANALYSIS

$$\begin{bmatrix} G_{11} & G_{12} & \cdots & G_{1n} \\ G_{21} & G_{22} & \cdots & G_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ G_{n1} & G_{n2} & \cdots & G_{nn} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_n \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_n \end{bmatrix}$$

$G_{kk} = \text{sum of all conductances } (\frac{1}{R})$  connected to node k


$G_{kl} = G_{lk} = \text{negative of conductance(s) connecting k/l}$

$V_k = \text{voltage at node k}$  [skip a node (=)]

$I_k = \text{total of current sources entering node k}$  (add current sources leaving node k as negative)

SOURCE TRANSFORMATION you know this buddy!

## Δ-Y TRANSFORMATION

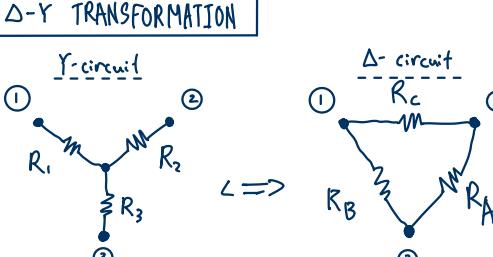

## Y → Δ

$$A = \frac{1+2+3+3 \cdot 1}{1}$$

$$B = \frac{1+2+3+3 \cdot 1}{2}$$

$$C = \frac{1+2+3+3 \cdot 1}{3}$$

$$\text{for } A=B=C \Rightarrow 1=2=3 = A/3$$


$$\text{for } R_1=R_2=R_3 \Rightarrow A=B=C=3 \cdot R_1$$

$$\begin{array}{l} \text{D} \rightarrow \text{Y} \\ I = \frac{RC}{A+B+C} \\ Z = \frac{AC}{A+B+C} \\ 3 = \frac{AB}{A+B+C} \end{array}$$

$$\text{for } A=B=C \Rightarrow 1=2=3 = A/3$$

$$\text{for } R_1=R_2=R_3 \Rightarrow A=B=C=3 \cdot R_1$$

## THEVENIN & NORTON EQUIVALENTS

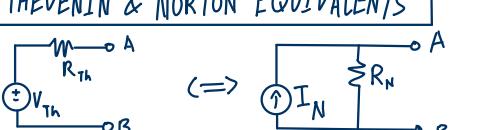

$$V_{Th} = V_A - V_B \text{ in open circuit}$$

$$R_{Th} = R_N \quad I_N = V_{Th} / R_{Th}$$

$$I_N = \text{current flowing from A to B in short}$$


$$R_{Th}: \text{short all } V \text{ sources}$$

$$\text{open all } I \text{ sources}$$

$$R_{Th} = R_N = V_{Th} / I_N$$

## WHEATSTONE BRIDGE

balanced + no approximation

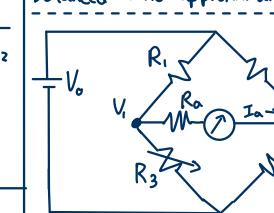


$$\Rightarrow \frac{R_2 V_0}{R_1 + R_2} = \frac{R_x V_0}{R_1 + R_x}$$

$$\text{and } \frac{R_1 V_0}{R_1 + R_3} = \frac{R_2 V_0}{R_2 + R_x}$$

$$\Rightarrow R_x = \left( \frac{R_2}{R_1} \right) R_3$$

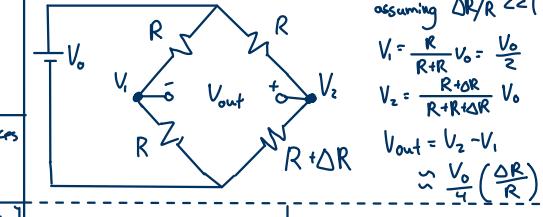sensor for small deviations from a ref. cond.



$$V_{out} = V_0 \cdot \frac{R}{R + \Delta R}$$

$$\approx \frac{V_0}{4} \left( \frac{\Delta R}{R} \right)$$

Capacitors:

$$i = C \frac{dv}{dt}$$

$$\omega = \frac{1}{2} C v^2$$

• v can't change instantly

• i CAN change instantly

• v can change instantly

Inductors:

$$v = L \frac{di}{dt}$$

$$\omega = \frac{1}{2} L i^2$$

• i can't change instantly

• v can change instantly

• i can't change instantly

• v can change instantly

$$V_{out}(t) = e^{-t/R} S_o e^{\frac{t}{RC}} \frac{V_{in}(t)}{RC}$$

$$V_{out} = V_o (1 - e^{-t/RC})$$

$$V_c(t=0^+) = V_c(t=0^-)$$

$$i_L(t=0^+) = i_L(t=0^-)$$

$$i_C(t=\infty) = C \frac{dV_c}{dt} = 0 \rightarrow \text{open}$$

$$V_L(t=\infty) = L \frac{di_L}{dt} = 0 \rightarrow \text{short}$$

capacitor @ t = 0+ → short

inductor @ t = 0+ → open

capacitor @ t = 0+ → short

inductor @ t = 0+ → open

works for voltage too

$$V_c(t=0^+) = V_c(t=0^-)$$

$$i_L(\infty) = C \frac{dV_c}{dt} = 0 \rightarrow \text{open}$$

$$i_L(t=0^+) = i_L(t=0^-)$$

$$V_L(\infty) = L \frac{di_L}{dt} = 0 \rightarrow \text{short}$$

## SUPERPOSITION PRINCIPLE



$$V_3 = I R_4 \quad \text{short } V \text{ open } I \text{ sources}$$

$$I = \frac{R_1}{R_{1+2+3+4}} I_{S1} + \frac{R_{1+2}}{R_{1+2+3+4}} I_{S2} + \frac{R_{1+2+3}}{R_{1+2+3+4}} I_{S3}$$

$$I = \frac{R_1}{R_{1+2+3+4}} I_{S1} + \frac{R_{1+2}}{R_{1+2+3+4}} I_{S2} + \frac{R_{1+2+3+4}}{R_{1+2+3+4}} I_{S4}$$

**CAPACITORS**

$$C = \frac{\epsilon A}{d} \quad \epsilon_0, \text{ permittivity of vacuum} = 8.854 \times 10^{-12} \text{ F/m}$$

$$Q = CV \quad \epsilon = \epsilon_r \epsilon_0$$

$$i = C \frac{dV}{dt} = C \frac{dQ}{dt}$$

$$V(t) = \frac{1}{C} \int_0^t i dt + V(t_0)$$



charging @  $t=0$

$$V_s - IR - V_c = 0$$

$$V_s - RC \frac{dV_c}{dt} - V_c = 0$$

$$V_s - V_c = RC \frac{dV_c}{dt}$$

$$\frac{1}{RC} dV_c = \frac{1}{V_s - V_c} dt$$

$$\int \frac{1}{V_c(t)} \frac{1}{V_s - V_c} = \int_0^t \frac{1}{RC} dt$$

$$-\ln(V_s - V_c(t)) + \ln(V_s - V_c(0)) = \frac{t}{RC}$$

$$= \ln\left(\frac{V_s - V_c(0)}{V_s - V_c(t)}\right) = \frac{t}{RC}$$

$$\ln\left(\frac{V_s - V_c(t)}{V_s - V_c(0)}\right) = -t/RC$$

$$\frac{V_s - V_c(t)}{V_s - V_c(0)} = e^{-t/RC}$$

$$V_s - V_c(t) = (V_s - V_c(0))e^{-t/RC}$$

$$V_c(t) = V_s - (V_s - V_c(0))e^{-t/RC}$$

$$V_c(t) = V_s(1 - e^{-t/RC})$$

$$\frac{1}{C_{\text{series}}} = \frac{1}{C_1} + \frac{1}{C_2} \quad C_{\text{parallel}} = C_1 + C_2$$

Power and energy

$$P(t) = V_i I$$



$$= V_c C \frac{dV_c}{dt}$$

$$\int_0^\infty P(t) dt = C \int_0^\infty V_c \frac{dV_c}{dt} dt$$

$$= \frac{1}{2} C V_c^2$$

$$W = \frac{1}{2} C V_c^2 \Rightarrow \text{stored in capacitor}$$

(energy)

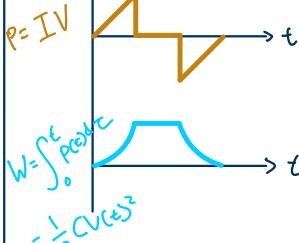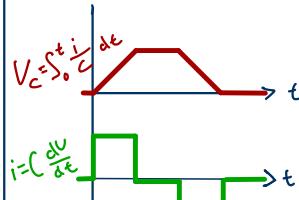

**INDUCTORS**

$$L = \frac{\mu N^2 S}{l}$$

$$i = \frac{dQ}{dt} \quad \mu_F = \frac{\mu}{M_0}$$

$$\int_0^t \frac{V_L}{L} dt = \int_{i(0)}^{i(t)} di$$

$$\frac{1}{L} \int_0^t V_L dt = i(t) - i(0)$$

$$i(t) = i(0) + \frac{1}{L} \int_0^t V_L dt$$

$$L_{\text{series}} = L_1 + L_2 \quad \frac{1}{L_{\text{parallel}}} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$Z_R = R, \quad Z_L = j\omega L, \quad Z_C = \frac{1}{j\omega C}$$

### Phasor Notation

Convert everything to cosine

$$\sin(x) = \cos(x - 90^\circ)$$

For each term:

$$8\cos(6^\circ - 45^\circ) = 8e^{j(-45^\circ)} = 8L - 45^\circ$$

$$8L - 45^\circ = 8(\cos(-45^\circ) + j\sin(-45^\circ)) = 5.66 - 5.66j$$

$$\text{Magnitude} = \sqrt{5.66^2 + (-5.66)^2}$$

$$= 8.00$$

Phase Angle:

Draw real vs. imag graph  $\theta = \tan^{-1}(-5.66/5.66) = -45^\circ$

Final phasor:  $8.00L - 45^\circ = 8e^{j-45^\circ}$

### Power Stored in Capacitors

$$P(t) = V_i I = V_c C \frac{dV_c}{dt}$$

$$\int_0^\infty P(t) dt = \int_0^\infty V_c C \frac{dV_c}{dt} dt = \frac{1}{2} C (V_s)^2 = \frac{1}{2} C V_s^2$$

$$\text{Time Constant} \quad \frac{V_s}{\tau = R_{\text{eq}} C_{\text{eq}}} \quad \frac{\text{Voltage to dB}}{dB = 20 \log_{10}(V)}$$



$$V = 10^{dB/20}$$

\* \* \* \*

$$\text{octave} = 500 - 1000$$

First order HP

Filter

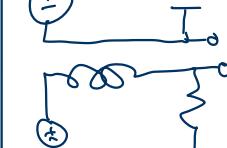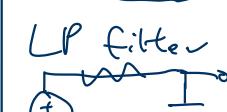

**INDUCTORS**

$$L = \frac{\mu N^2 S}{l}$$

$$i = \frac{dQ}{dt} \quad \mu_F = \frac{\mu}{M_0}$$

$$\int_0^t \frac{V_L}{L} dt = \int_{i(0)}^{i(t)} di$$

$$\frac{1}{L} \int_0^t V_L dt = i(t) - i(0)$$

$$i(t) = i(0) + \frac{1}{L} \int_0^t V_L dt$$

$$L_{\text{series}} = L_1 + L_2 \quad \frac{1}{L_{\text{parallel}}} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$Z_R = R, \quad Z_L = j\omega L, \quad Z_C = \frac{1}{j\omega C}$$

**TRANSFER FUNCTIONS**

$$N = \# \text{ coils}$$

$$S = \text{cross-sectional area}$$

$$\mu_0 = 4\pi \cdot 10^{-7} \text{ H/m}$$

### BODE PLOTS

1st order: denominator has  $w$  deg 1

$$|H_1(\omega_c)| = \frac{1}{\sqrt{2}} \text{ of max } |H_1(\omega)|$$


filter roll off:  $\pm 20 \text{ dec/dB}$

$$|H_2(\omega_c)| = \frac{1}{2} \text{ of max } |H_2(\omega)|$$

filter roll off =  $\pm 40 \text{ dec/dB}$

$$\angle H(\omega) = \angle H_{\text{numer}}(\omega) - \angle H_{\text{denom}}(\omega)$$
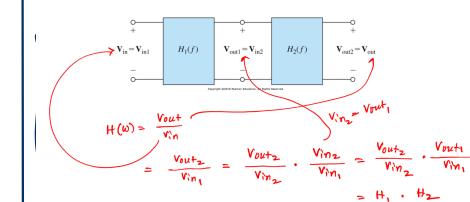
$$\angle H(\omega_c) = 90^\circ \text{ always}$$



$$20 \log(\omega^2) = 40 \log(\omega)$$

$$20 \log(\omega RL) = 20 \log(RL) + 20 \log(\omega)$$

$$20 \log\left(\frac{A}{B}\right) = 20 \log A - 20 \log B$$

Factor	Bode Magnitude	Bode Phase
Constant $K$	$20 \log K$ $\text{dB}$	$0^\circ - 90^\circ \pm 180^\circ$ if $K < 0$ $0^\circ (90^\circ)$ if $K > 0$
zero @ Origin $(j\omega)^N$	$0 \text{ dB}$	$(90N)^\circ$
Pole @ Origin $(j\omega)^{-N}$	$0 \text{ dB}$	$(-90N)^\circ$
Simple Zero $(1 + j\omega/\omega_c)^N$	$0 \text{ dB}$ at $\omega_c$ slope = $20N \text{ dB/dec}$	$(90N)^\circ$ at $\omega_c$ $0^\circ$ at $0.1\omega_c$ , $\omega_c$ , $10\omega_c$
Simple Pole $(\frac{1}{1 + j\omega/\omega_c})^N$	$0 \text{ dB}$ at $\omega_c$ slope = $-20N \text{ dB/dec}$	$0^\circ$ at $0.1\omega_c$ , $\omega_c$ , $10\omega_c$ $(-90N)^\circ$
Quadratic zero $[1 + j2\omega/\omega_c + (j\omega/\omega_c)^2]^N$	$0 \text{ dB}$ at $\omega_c$ slope = $40 \text{ dB/dec}$	$0^\circ$ at $0.1\omega_c$ , $\omega_c$ , $10\omega_c$ $(180N)^\circ$
Quadratic Pole $\frac{1}{[1 + j2\omega/\omega_c + (j\omega/\omega_c)^2]^N}$	$0 \text{ dB}$ at $\omega_c$ slope = $-40 \text{ dB/dec}$	$0^\circ$ at $0.1\omega_c$ , $\omega_c$ , $10\omega_c$ $(-180N)^\circ$

## Second-Order DEs:

$$\frac{d^2x(t)}{dt^2} + 2\alpha \frac{dx(t)}{dt} + \omega_0^2 x(t) = 0$$

- $\alpha$ : Damping Factor
- $\omega_0$ : Undamped Natural Frequency

Characteristic Polynomial:

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

Homogeneous Solution:

$$x_h(t) = A e^{s_1 t} + B e^{s_2 t}$$

$$s_1 = -\alpha + i\sqrt{\alpha^2 - \omega_0^2}, s_2 = -\alpha - i\sqrt{\alpha^2 - \omega_0^2}$$

1. [Overdamped]:  $\alpha > \omega_0 \rightarrow s_1, s_2$  are real and neg.

$$x_h(t) = A e^{-(\alpha - \sqrt{\alpha^2 - \omega_0^2})t} + B e^{-(\alpha + \sqrt{\alpha^2 - \omega_0^2})t}$$

2. [Underdamped]:  $\alpha < \omega_0 \rightarrow s_1, s_2$  are complex

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$x_h(t) = e^{-\alpha t} [C \cos(\omega_d t) + D \sin(\omega_d t)]. \text{ (decaying sinusoid)}$$

3. [Critically Damped]  $\alpha = \omega_0 \rightarrow s_1 = s_2 = -\alpha$

$$x_h(t) = A e^{-\alpha t} + B t e^{-\alpha t}$$

Particular Solution


$$x_p(t) = X(t = \infty)$$

General Solution

$$x(t) = x_h(t) + x_p(t)$$


use  $x(0), x'(0)$  to solve for  $A, B, C, D$
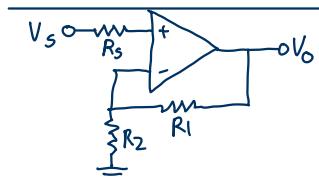
$$\begin{aligned} A \cos(Cwt - x) &\quad (\star\star\star) \\ = -A \cos(Cwt - x + 180^\circ) &\quad (A < B^\circ) (C < 0^\circ) \\ = -A \cos(Cwt - (x - 180^\circ)) &\quad = (A C) < (B^\circ + 10^\circ) \end{aligned}$$




Non-inverting Amp  
(Vo independent of Rs)
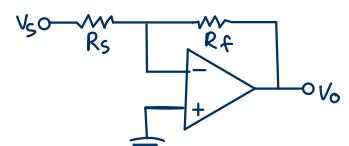
$$V_s \rightarrow G = \frac{R_1 + R_2}{R_2} \rightarrow V_o = G V_s$$



$$V_s \rightarrow G = -\frac{R_f}{R_1} \rightarrow V_o = G V_s$$


Inverting Amp

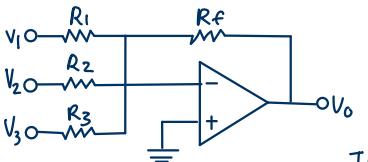

Inverting Summing Amp

$$V_1 \rightarrow G_1 = -\frac{R_2}{R_1}, V_2 \rightarrow G_2 = -\frac{R_3}{R_2}, V_3 \rightarrow G_3 = -\frac{R_4}{R_3}$$

$$V_o = G_1 V_1 + G_2 V_2 + G_3 V_3$$

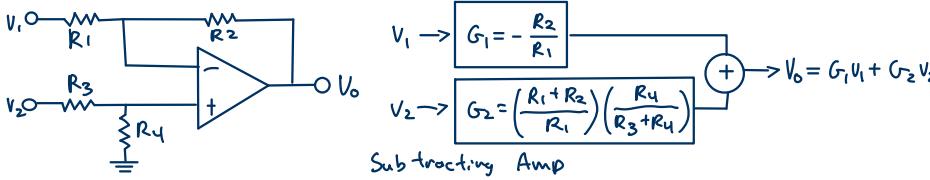


Subtracting Amp

$$V_1 \rightarrow G_1 = -\frac{R_2}{R_1}, V_2 \rightarrow G_2 = \frac{(R_1 + R_2)}{(R_3 + R_4)}, V_o = G_1 V_1 + G_2 V_2$$




Voltage Follower/Buffer  
(Vo independent of Rs & Rf)
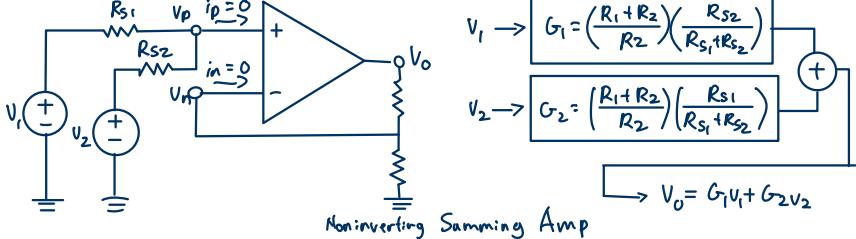
$$\rightarrow G = 1 \rightarrow V_o = V_s$$




Non-inverting Summing Amp
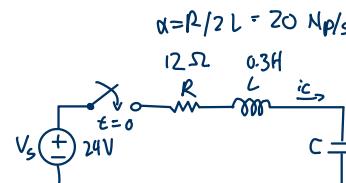
$$V_1 \rightarrow G_1 = \frac{(R_1 + R_2)}{R_2}, V_2 \rightarrow G_2 = \frac{(R_1 + R_2)}{R_1}, V_o = G_1 V_1 + G_2 V_2$$




$$\alpha = R/2L = 20 \text{ Np/s}$$

② charging up C

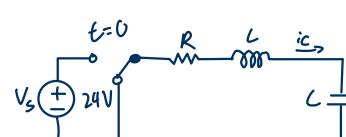



③ Discharging C

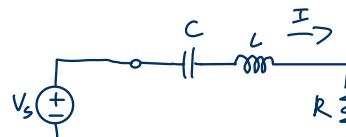RLC circuit with  $V_o$  on R: Bandpass filter



$$I = \frac{V_s}{R + j(wL - \frac{1}{wC})}$$

$$= \frac{jwCV_s}{(1 - w^2LC) + jwRC}$$

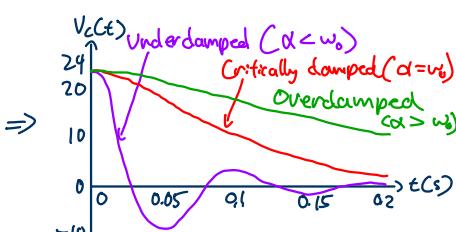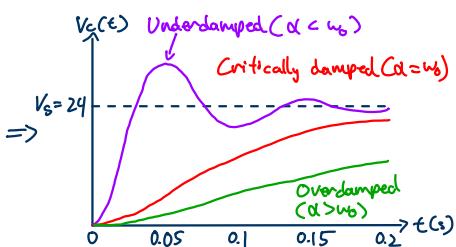

$$H(\omega) = \frac{V_R}{V_s} = \frac{R I}{V_s}$$

$$= \frac{jwRC}{(1 - w^2LC) + jwRC}$$

$$|H(\omega)| = \frac{wRC}{\sqrt{(1 - w^2LC)^2 + w^2R^2C^2}}$$

$$\beta(\omega) = 90^\circ - \tan^{-1}\left[\frac{wRC}{1 - w^2LC}\right]$$

$$\omega_0 = 1/\sqrt{LC}$$

$$\omega_{C1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$


$$\omega_{C2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$


$$\beta = \omega_{C2} - \omega_{C1} = \frac{R}{L} \quad \omega_0 = \sqrt{\omega_{C1} \omega_{C2}}$$

$$Q = \frac{\omega_0 L}{R} = \frac{\omega_0}{B} \quad M_{BP}[\text{dB}]$$

$$Q = 2\pi \left( \frac{W_{Star}}{W_{Diss}} \right) \quad @ \omega = \omega_0$$

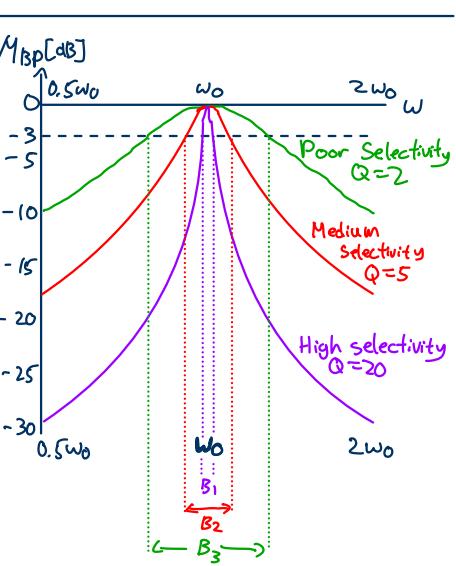High Q = high selectivity & narrow bandwidth




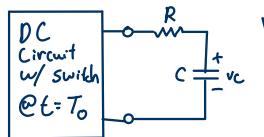

$$V_c(t) = V_c(\infty) + [V_c(T_0) - V_c(\infty)]e^{-(t-T_0)/\tau}$$

$$\tau = R_{eq} C$$

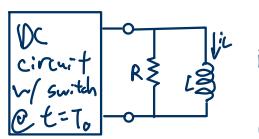
$$i_c(t) = \frac{1}{R} [V_c(T_0) - V_c(\infty)] e^{-(t-T_0)/\tau}$$




$$i_L(t) = i_L(\infty) + [i_L(T_0) - i_L(\infty)] e^{-(t-T_0)/\tau}$$

$$\tau = L/R_{eq}$$
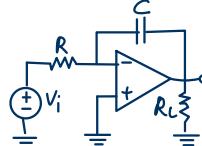
$$V_L(t) = -R [i_L(T_0) - i_L(\infty)] e^{-(t-T_0)/\tau}$$


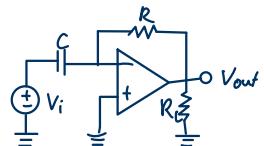
$$V_{out}(t) = -\frac{1}{RC} \int_{t_0}^t V_i dt + V_{out}(t_0)$$





$$V_{out}(t) = -RC \frac{dV_i}{dt}$$



+/- in n/p indicates extent of doping.  
N+ means heavily doped

nFet; pFet  $\rightarrow$  swap

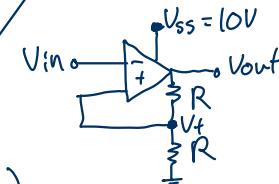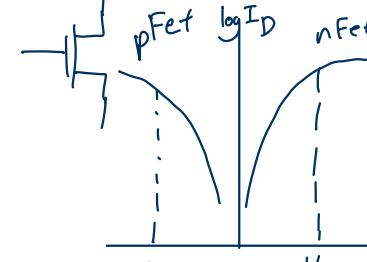



$$I_D = A e^{\frac{BV_D}{kT}} \quad (\text{exp before } V_T)$$

$$I_D = C(V_g - V_T)^2$$

(quad. after  $V_T$ )

ideal op amp characteristics

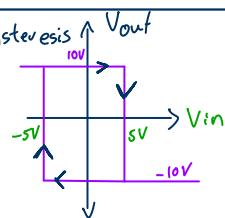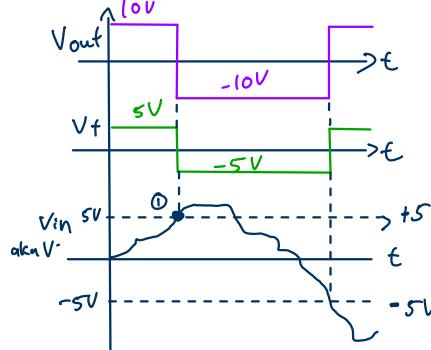
- $i_p = i_n = 0$
- $v_p = v_n$
- $A = \infty$
- $R_i = \infty$
- $R_o = 0$



- $V \rightarrow V_f$   
 $V_{out} = A(V_f - V) < 0$   
Vout and  $V_f$  flip sign  
As long as  $V > -5V$ ,  $V_f - V < 0$   
if  $V_{in}$  goes under  $-5V$ .
- $V_f - V > 0 \rightarrow V_{out} & V_f$  flip sign again


ideal op amp characteristics

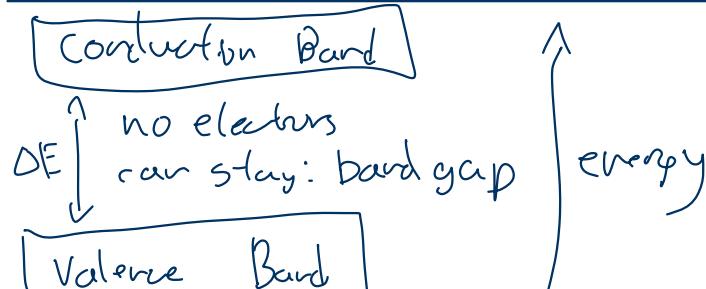- $i_p = i_n = 0$
- $v_p = v_n$
- $A = \infty$
- $R_i = \infty$
- $R_o = 0$



Smaller band gap  $\rightarrow$  more conductive

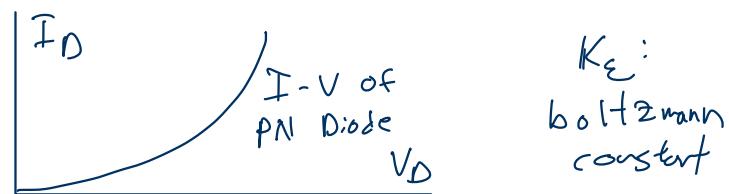$P(\text{electron at } C \text{ band due to thermal energy}) \sim e^{-\Delta E/kT}$




$K_E$ : Boltzmann constant

N-type material: extra electrons added to conduction band from donor material (phosphorus for silicon)

p-type material: atoms with one fewer valence electron used to dope the silicon creates holes in conduction band

p-side n-side  
diode

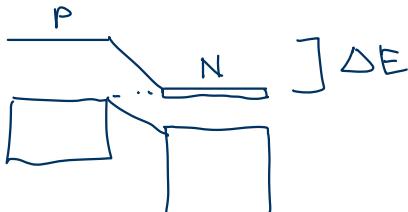

$\text{forward bias}$

$V_D > 0$   
 $\rightarrow \Delta E' < \Delta E$

$\text{reverse bias}$

$V_D < 0$   
 $\Delta E' > \Delta E$

#### Quality factor

According to the foregoing discussion, the choice of values we make for  $R$ ,  $L$ , and  $C$  will specify the overall shape of the transfer function completely, as well as its center frequency  $\omega_0$  and bandwidth  $B$ .

► The **quality factor** of a circuit  $Q$  is an attribute commonly used to characterize the **degree of selectivity** of the circuit. A high  $Q$  circuit has a narrow bandwidth (relative to the center frequency) and high selectivity. ▶

**Figure 9-16** displays frequency responses for three circuits, all with the same  $\omega_0$ . The high- $Q$  circuit exhibits a sharp response with a narrow bandwidth (relative to  $\omega_0$ ), the medium- $Q$  circuit has a broader pattern, and the low- $Q$  circuit has a pattern with limited selectivity.

For the bandpass-filter response,  $Q$  obviously is related to the ratio  $\omega_0/B$ , but the formal definition of  $Q$  applies to any resonant circuit and is based on energy considerations, namely

$$Q = 2\pi \left( \frac{W_{\text{stor}}}{W_{\text{diss}}} \right) \Big|_{\omega=\omega_0}, \quad (9.53)$$

Upon substituting Eqs. (9.59) and (9.60) into Eq. (9.53), we obtain the result

$$Q = \frac{\omega_0 L}{R} \quad (\text{bandpass filter}).$$

Using the relation given by Eq. (9.51), the expression for quality factor becomes

$$Q = \frac{\omega_0}{B} \quad (\text{bandpass filter}),$$

The current  $I$  flowing through the loop in Fig. 9-15(a) is given by

$$I = \frac{V_s}{R + j \left( \omega L - \frac{1}{\omega C} \right)} = \frac{j\omega CV_s}{(1 - \omega^2 LC) + j\omega RC}, \quad (9.44)$$

where we multiplied the numerator and denominator by  $j\omega C$  to simplify the form of the expression. The transfer function corresponding to  $V_R$  is

$$H_{\text{BP}}(\omega) = \frac{V_R}{V_s} = \frac{RI}{V_s} = \frac{j\omega RC}{(1 - \omega^2 LC) + j\omega RC}, \quad (9.45)$$

where we added the subscript "BP" in anticipation of the fact that  $H_{\text{BP}}(\omega)$  is the transfer function of a bandpass filter. Its magnitude and phase angle are given by

$$M_{\text{BP}}(\omega) = |H_{\text{BP}}(\omega)| = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}}, \quad (9.46)$$

and

$$\phi_{\text{BP}}(\omega) = 90^\circ - \tan^{-1} \left[ \frac{\omega RC}{1 - \omega^2 LC} \right]. \quad (9.47)$$

$$M_{\text{BP}}^2(\omega) = \frac{1}{2} \quad @ \omega_{c_1} \text{ and } \omega_{c_2}. \quad (9.49)$$

Upon inserting the expression for  $M_{\text{BP}}(\omega)$  given by Eq. (9.46) and carrying out several steps of algebra, we obtain the solutions

$$\omega_{c_1} = -\frac{R}{2L} + \sqrt{\left( \frac{R}{2L} \right)^2 + \frac{1}{LC}} \quad (9.50a)$$

and

$$\omega_{c_2} = \frac{R}{2L} + \sqrt{\left( \frac{R}{2L} \right)^2 + \frac{1}{LC}}. \quad (9.50b)$$

The bandwidth then is given by

$$B = \omega_{c_2} - \omega_{c_1} = \frac{R}{L}. \quad (9.51)$$

It is worth noting that  $\omega_0$  is equal to the geometric mean of  $\omega_{c_1}$  and  $\omega_{c_2}$ :

$$\omega_0 = \sqrt{\omega_{c_1} \omega_{c_2}}. \quad (9.52)$$

Table 9-5: Response forms of basic first-order circuits.		
Circuit	Diagram	Response
RC		$v_c(t) = [v_c(\infty) + (v_c(T_0) - v_c(\infty))e^{-(t-T_0)/\tau}] + v(t-T_0) \quad (\tau = RC)$
RL		$i_L(t) = [i_L(\infty) + (i_L(T_0) - i_L(\infty))e^{-(t-T_0)/\tau}] + v(t-T_0) \quad (\tau = L/R)$
Ideal integrator		$v_{\text{out}}(t) = -\frac{1}{RC} \int v_s dt + v_{\text{out}}(0)$
Ideal differentiator		$v_{\text{out}}(t) = -RC \frac{dv_s}{dt}$

(9.52)

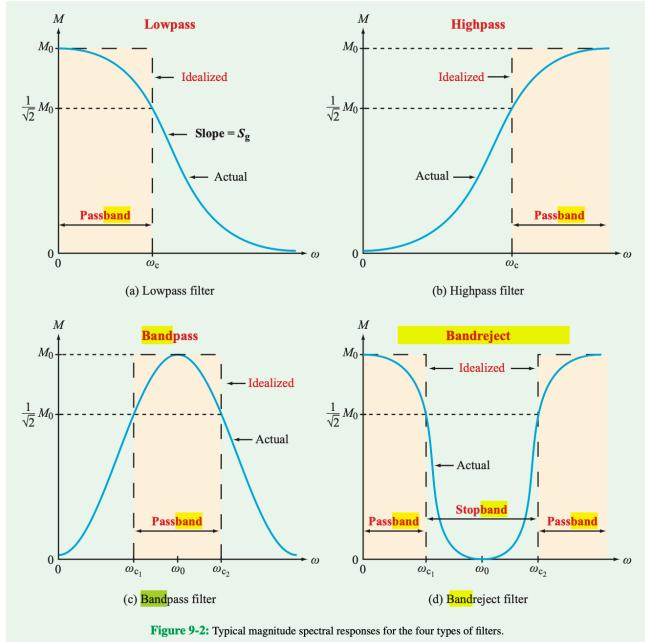


Figure 9-2: Typical magnitude spectral responses for the four types of filters.



finding diff eq in terms of  $i_L(t)$

$$\begin{aligned} i_s &= i_R + i_L + i_C \\ &= \frac{V_R}{R} + i_L + C \frac{dV_C}{dt} \\ &= \frac{V_L}{R} + i_L + C \frac{dV_C}{dt} \\ i_s &= \frac{L}{R} \frac{di_L}{dt} + i_L + CL \frac{d^2 i_L}{dt^2} \end{aligned}$$

to standard form

$$i_L'' + \frac{1}{RC} i_L' + \frac{1}{LC} i_L = \frac{1}{LC} i_s$$

determining initial conditions

$$i_L(0^+): i_L(0^+) = i_L(0^-) = 0$$

$i_L'(0^+)$ :  $i_L'(0^+) = 0$  since all current flows through the capacitor, which acts as short

$i_L(\infty)$ :  $I_s$  since all current will flow through inductor, which acts as short

solving for  $i_L(t)$

solve for homogeneous soln

$$i_L'' + \frac{1}{RC} i_L' + \frac{1}{LC} i_L = 0$$

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

$$2\alpha = \frac{1}{RC} \quad \omega_0^2 = \frac{1}{LC}$$

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

assuming  $R < 5$

$$C = 1 \mu F$$

$$L = 1 \mu H$$

$$\alpha = 10^5 \quad \omega_0 = 10^9$$

$\alpha < \omega_0 \Rightarrow$  under damped

$$x_h(t) = e^{-\alpha t} (C \cos(\omega_d t) + D \sin(\omega_d t))$$

solve for  $C$  &  $D$

$$i_L(0) = e^0 (C + 0)$$

$$= C = 0$$

$$\begin{aligned} x_h'(t) &= -\alpha e^{-\alpha t} (\cos(\omega_d t) + e^{-\alpha t} C \omega_d (-\sin(\omega_d t))) \\ &\quad - \alpha e^{-\alpha t} D \sin(\omega_d t) + e^{-\alpha t} D \omega_d \cos(\omega_d t) \end{aligned}$$

$$x_h(0) = -\alpha(1)C(1) + \cancel{(-1)C \omega_d(0)}$$

$$\cancel{-\alpha(1)D(0)} + (1)D\omega_d(1)$$

$$= -\alpha C + \omega_d D$$

now soln is homogeneous soln + particular soln

$$X = X_h + X_p \quad X_p = X(\infty) = i_L(\infty) = I_s$$

$$i_h(t) = A e^{-(\alpha - \sqrt{\alpha^2 - \omega_0^2})t} + B e^{-(\alpha + \sqrt{\alpha^2 - \omega_0^2})t}$$

$$i'_h(t) = -(\alpha - \omega_d) A e^{-(\alpha - \omega_d)t} - (\alpha + \omega_d) B e^{-(\alpha + \omega_d)t}$$

$$\begin{aligned} i'_h(0) &= -(\alpha - \omega_d)A - (\alpha + \omega_d)B \\ &= (\omega_d - \alpha)A - (\omega_d + \alpha)B \end{aligned}$$

